

Schematics (Out = A1.A2.A3 + B1.B2.B3)

 

 





Complex logic Layout

 Area \Rightarrow 2.4um x 2.2um \Rightarrow 5.28 um^2






Without NP & PP Layers

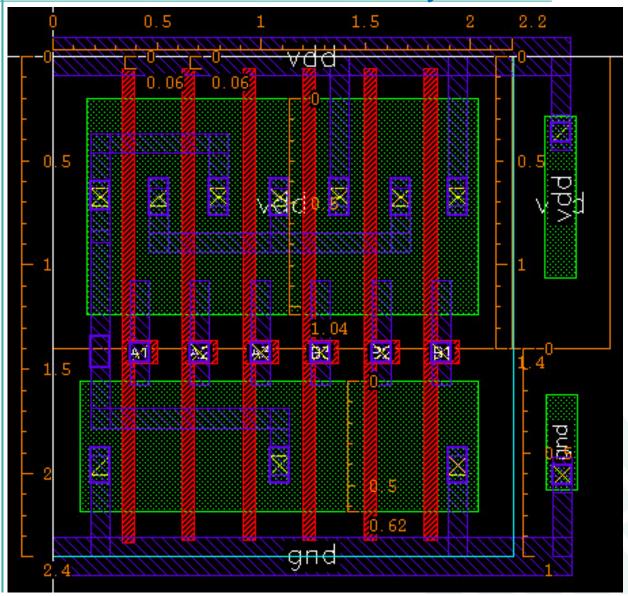


Non-Complex Logic Layout with all layers



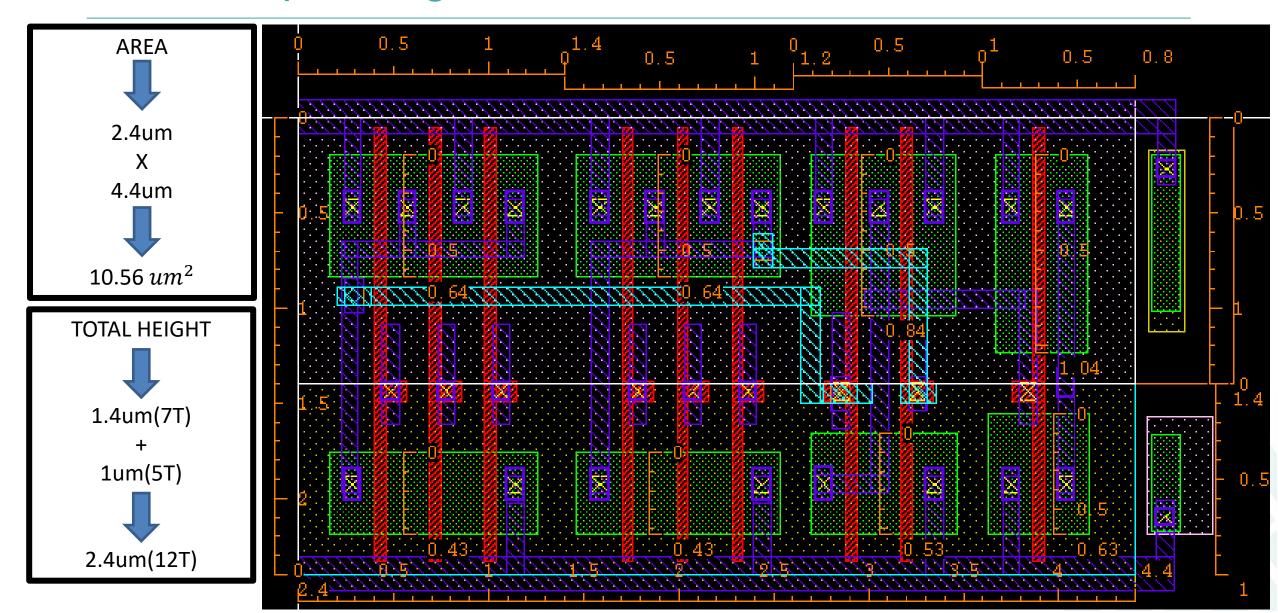

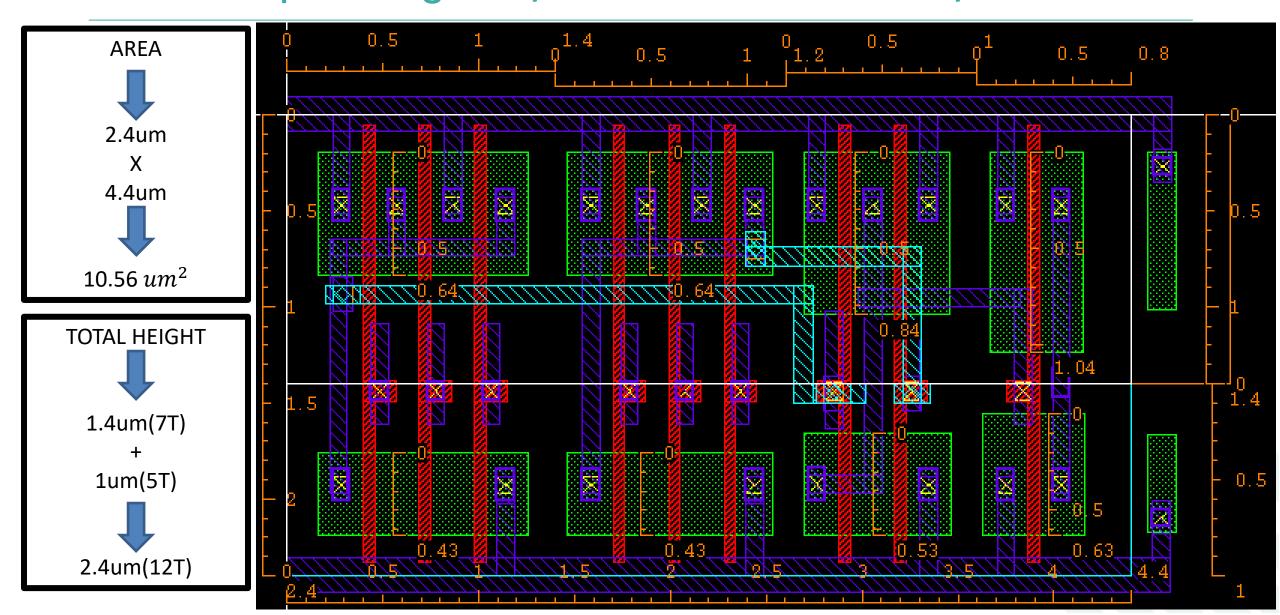Non-Complex Logic Layout without NP & PP layers






Simulation Waveforms (Ezwave)

Complex logic

Non Complex logic




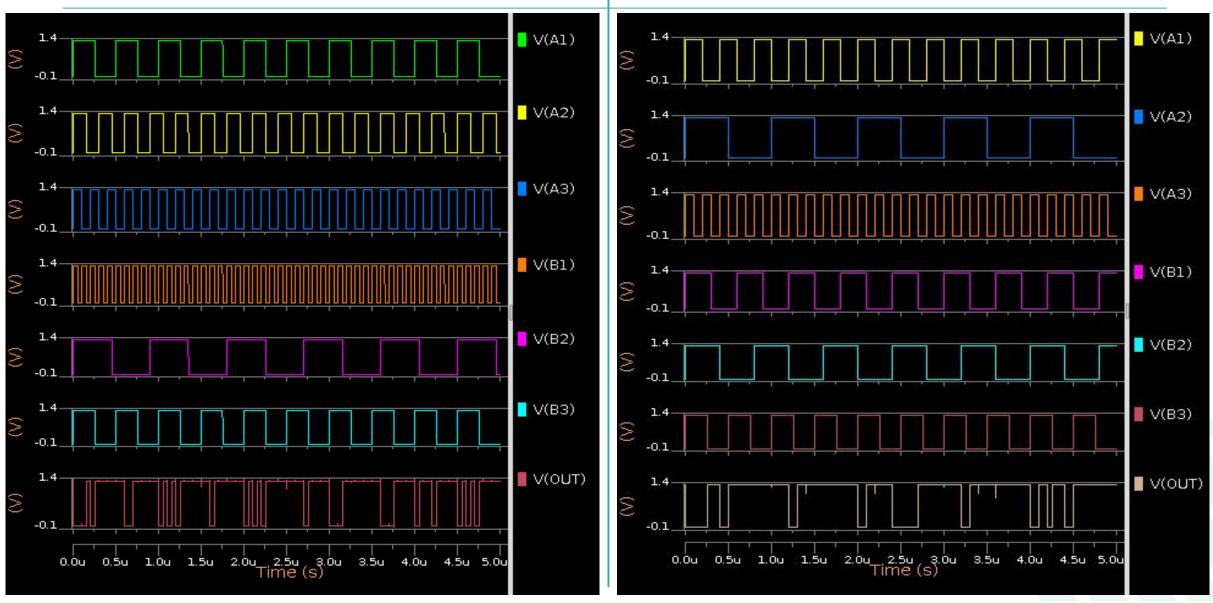


DRC, LVS and PEX Results





 

Non Complex Logic

 

Simulation Results and Comparison



| PARAMETERS | PVT CONDITION | COMPLEX LOGIC | | NON COMPLEX LOGIC | |
|------------|------------------|---------------|------------|-------------------|------------|
| | (Worst Case) | PRELAYOUT | POSTLAYOUT | PRELAYOUT | POSTLAYOUT |
| TPDR | SS, 125°C, 1.08V | 151ps | 203ps | 206ps | 200ps |
| TPDF | SS, 125°C, 1.08V | 360ps | 292ps | 232ps | 222ps |
| TCDR | FF, -40°C, 1.32V | 37.3ps | 38.2ps | 71.3ps | 72.2ps |
| TCDF | FF, -40°C, 1.32V | 48.6ps | 45.4ps | 76.9ps | 76.9ps |
| TRISE | SS, 125°C, 1.08V | 273ps | 259ps | 130ps | 132ps |
| TFALL | SS, 125°C, 1.08V | 408ps | 329ps | 113ps | 110ps |
| ILEAK | FF, 125°C, 1.32V | 60.2nA | 63.3nA | 101nA | 157nA |
| PDYN | TT, 25°C, 1.2V | 50.1nW | 48.2nW | 62.2nW | 90.4nW |
| PSTATIC | TT, 25°C, 1.2V | 443pW | 568pW | 644pW | 709pW |

| PARAMETER | COMPLEX LOGIC | NON COMPLEX LOGIC | |
|-----------|----------------------|-------------------|--|
| AREA | 5.28 um ² | 10.56 um^2 | |

PPA, Comparison and Conclusion



POWER – Power of Non Complex logic is observed to be more than Complex logic. Power of Post layout simulation is more than Pre layout simulation in both the logics.

PERFORMANCE – For both pre and post layout simulations, the delays for the Complex logic are slightly less than the Non Complex logic. The analysis has been performed under the worst case of PVT condition, so our proposed circuit will work well under all other PVT conditions.

AREA – Area of Complex logic(5.28 um^2) is half of the area of Non Complex logic(10.56 um^2).

LEARNINGS



- 1. Making layout from scratch (without generating from source).
- 2. About pc_ct pins (to restrict short circuiting).
- 3. Sizing beyond theoretical calculation (logical effort).
- 4. The circuits will be fast for high voltage and low temp. Slow for low voltage and high temperature.
- 5. Learning about standard cells (DRC's like Poly head to head DRC)
- 6. Use of M2 for routing.
- 7. Tradeoff between delays and leakage.
- 8. Better layouts may lead to reduced delays after PEX.
- 9. Area is Gold!!